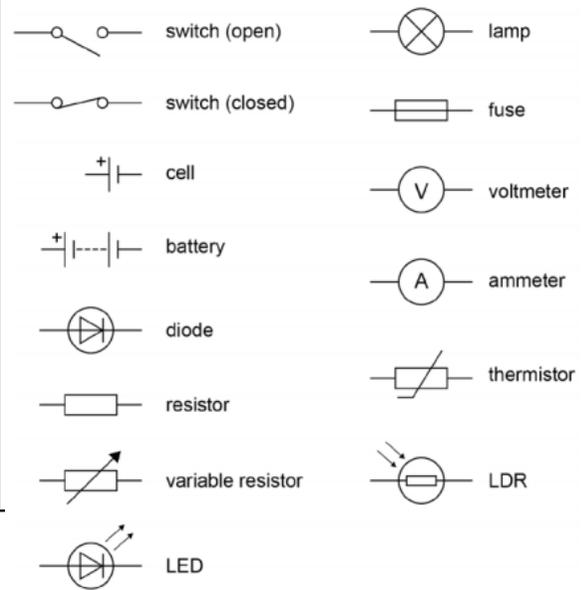


6.2 Electricity


Section 1: Circuit Diagram symbols

Circuit diagrams use standard symbols.




Section 2 Electrical Charge

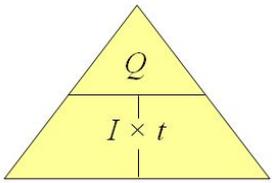- Charge flow = current x time
- charge flow (Q): in **coulombs (C)**
- Current (I): in **amperes (A)**
- Time (t): in **seconds (s)**
- A current has the **same** value at any point in a single closed loop




Section 3 Current, resistance and potential difference.

- The **current (I)** through a component depends on both the **resistance (R)** of the component and the **potential difference (V)** across the component.
- The greater the resistance** of the component the **smaller the current** for a given potential difference (pd) across the component.
- potential difference = current x resistance
- (V = I R)**
- potential difference (V): in **volts (V)**
- Current (I): in **amperes (A)**
- Resistance (R): in **ohms (Ω)**

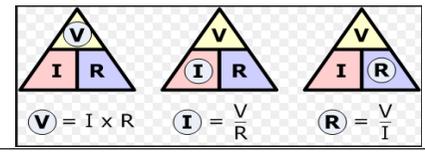


Section 4a) Resistance Required Practical - Resistance of a wire varying by length

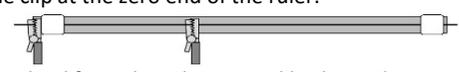- Connect a lead from the **positive** socket of power pack to the positive side of the **ammeter**.
- Connect a lead from the **negative** side of the **ammeter** (this may be black) to the crocodile clip at the zero end of the ruler.





- Connect a lead from the other crocodile clip to the negative side of the **battery**.
- The main loop of the circuit is now complete. Use this lead as a switch to disconnect the battery between readings.
- Connect a lead from the positive side of the **voltmeter** to the crocodile clip the **ammeter** is connected to.
- Connect a lead from the negative side of **the voltmeter** to the other crocodile clip.
- Record on a table the: **length of the wire between the crocodile clips, the readings on the ammeter, the readings on the voltmeter.**
- Move crocodile clip and record the **new ammeter and voltmeter readings.**
- Repeat for **different** lengths of wire.
- Calculate and record** the resistance for each length of wire using the equation:

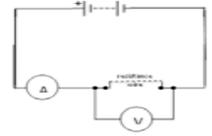

$$\text{resistance in } \Omega = \frac{\text{potential difference in V}}{\text{current in A}}$$

Section 4b Resistance Required Practical – Resistors in Series and Parallel

- Connect the circuit for **two resistors in series**, as shown in the diagram.
- Switch on and record the readings on the **ammeter** and the **voltmeter**.
- Use these readings to **calculate** the **total resistance** of the circuit.
- Now set up the circuit for **two resistors in parallel**. Switch on and record the readings on the **ammeter** and the **voltmeter**.
- Use these readings to **calculate** the **total resistance** of the circuit.
- With one single resistor in the circuit, the total resistance would be 10 ohms. What is the effect on the total resistance of adding:
another **identical resistor in series**
another **identical resistor in parallel**?
- You could also try setting up a circuit with three resistors in series and one with three resistors in parallel.

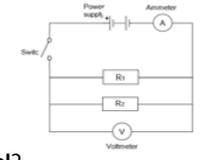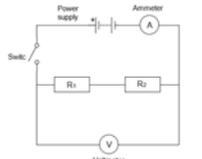

Section 5: Rules of series and parallel circuits

- For components connected in **series**:
- there is the **same current** through each component
 - the total **potential difference** of the power supply is **shared** between the components
 - the **total resistance** of two components is the **sum** of the resistance of **each** component.
- $$R_{\text{total}} = R_1 + R_2$$
- Resistance (R): in **ohms (Ω)**
- For components connected in **parallel**:
- the **potential difference** across each component is the **same**
 - the total **current** through the whole circuit is the **sum** of the currents through the **separate** components
 - the **total resistance** of two resistors is **less than** the resistance of the **smallest** individual resistor.

Section 6: Direct and Alternating Current


Mains electricity is an ac supply.
In the United Kingdom the domestic electricity supply has a frequency of 50 Hz and is about 230 V.
Direct current flows in one direction only.
Alternating current constantly changes direction.

6.2 Electricity

Section 7: Resistors


For some resistors, the value of R remains **constant**.

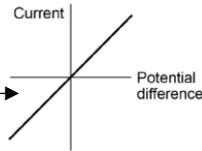The current through a conductor is **directly proportional** to the potential difference across the resistor. This means that the **resistance remains constant** as the **current** changes.




In other components, resistance can change as the current changes.

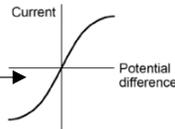The **resistance** of a filament lamp **increases** as the **temperature** of the filament **increases**.



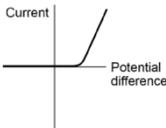The current through a **diode** flows in one direction only. The diode has a very **high** resistance in the **reverse** direction.




The resistance of a **thermistor** **decreases** as the **temperature** **increases**.

The resistance of an **LDR** **decreases** as **light intensity** **increases**.

Section 8: Required Practical: Current and Potential Difference Characteristics.


Resistor

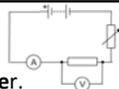1. Connect the circuit.
2. Record readings on the **ammeter** and **voltmeter**.
3. Adjust **variable resistor** and record the new ammeter and voltmeter readings. **Repeat** to obtain several pairs of readings.
4. **Swap** connections on the battery. Now the **ammeter** is connected to the **negative terminal** and the **variable resistor** to the **positive**. The readings on the ammeter and voltmeter should now be **negative**.
5. Continue to record readings of **current** and **potential difference**.
6. Plot graph with: 'Current in A' on y-axis, 'Potential difference in V' on x-axis.
7. You should be able to draw a **straight** line of best fit through the **origin**. This is the **characteristic of a resistor**.




Lamp

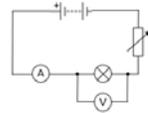1. Connect the circuit.
2. The lamp will get **hot**. Take care not to touch it.
3. Follow the same steps as for using a resistor.
6. Plot graph with: 'Current in A' on y-axis, 'Potential difference in V' on x-axis.
7. The **origin** will be in the **middle** of paper. Draw a **curved** line of best fit for your points.



Diode

1. Connect the circuit, adding in a **milliammeter**.
2. Reduce the battery potential difference to **less than 5V**.
3. Follow the same steps as for using a resistor.
6. Plot graph with: 'Current in A' on y-axis, 'Potential difference in V' on x-axis.
7. The **origin** will probably be in the **middle of the bottom** of your graph paper. There should **not** be any **negative** values of current.

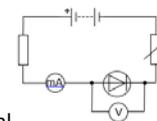

Section 9: Mains electricity

Most electrical **appliances** are connected to the **mains** using **three-core cable**.

The insulation covering each wire is colour coded for easy identification:

live wire – brown

neutral wire – blue

earth wire – green and yellow stripes.

The **live wire** carries the **alternating potential difference** from the supply. The **neutral wire** **completes** the circuit. The **earth wire** is a **safety wire** to stop the appliance becoming live.

The **potential difference** between the **live wire** and **earth** (0 V) is about **230 V**. The **neutral wire** is at, or close to, earth potential (**0 V**). The earth wire is at 0 V, it only carries a current if there is a **fault**. A live wire may be **dangerous** even when a switch in the mains circuit is open.

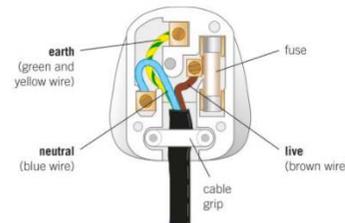


Figure 2 Inside a three-pin plug

Section 10: Power

1. The **power transfer** in any circuit device is related to the potential difference across it and the **current** through it, and to the energy changes over **time**:
 2. power = potential difference × current
 3. **(P = V I)**
 4. power = current² × resistance
 5. **(P = I² R)**
- Power (P): **in watts (W)**
 potential difference (V): **in volts (V)**
 Current (I): **in amperes (A)**
 Resistance (R): **in ohms (Ω)**

Section 11: Energy Transfer

1. Everyday **electrical appliances** are designed to bring **about energy transfers**.
2. The amount of energy an appliance transfers depends on **how long** the appliance is switched on for and the **power** of the appliance
3. **Work is done** when **charge flows** in a circuit
4. The amount of **energy transferred** by electrical work can be calculated using the equation: energy transferred = power × time
5. **E = P t**
6. energy transferred = charge flow × potential difference
7. **E = Q V**
8. energy transferred (E): **in joules (J)**
9. Power (P): **in watts (W)**
10. Time (t): **in seconds (s)**
11. charge flow (Q): **in coulombs (C)**
12. potential difference (V): **in volts (V)**

Section 12: The National Grid

1. The **National Grid** links power stations to **consumers**.
2. Electrical **power** is **transferred** from power stations to consumers using the National Grid.
3. **Step-up transformers** are used to **increase the potential difference** from the power station to the transmission cables
4. **Step-down transformers** are used to **decrease**, to a much lower value, the **potential difference** for domestic use.
5. The National Grid is an **efficient** way to transfer energy because it uses a **large** potential difference. Therefore **less** current is used to transfer **power**.
6. Power loss due to the **resistance** heating in the cables is **much reduced**.